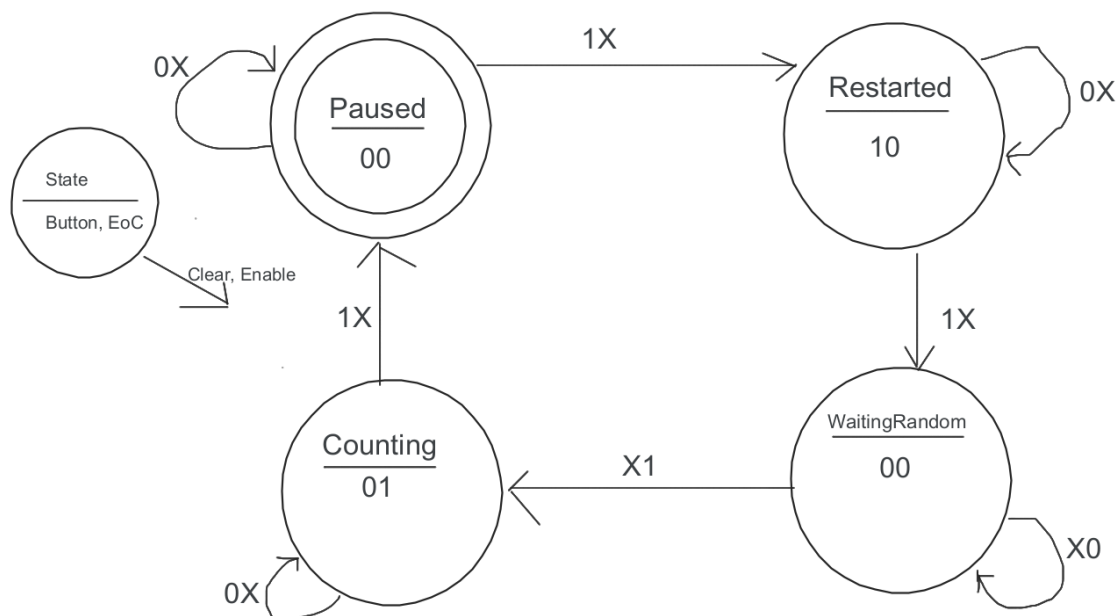


Finite State Machine



A Moore Diagram was used to represent FSM of the reaction timer system. Each state either enables a single input output of the FSM - the Clear or Enable to cause the display to clear or start counting, respectively. The inputs of the FSM are the button which is a direct input to the reaction timer system based on whether the user has pressed the button, and the EoC which is an output of an instance of a random timer to trigger the timer to start counting again.

The screenshot displays a logic analyzer interface with the following components:

- Signal List (Left):** A list of signals including MAX_COUNT, OUT_MAX[3:0], Reset, Clk, Enable, an[3:0], [3], [2], [1], [0], seg[6:0], CounterEnable, CounterValueMs[3:0], CounterVal...ths[3:0] (highlighted), CounterVa...onds[3:0], SecondsEnable, TenthsEnable, HundredthsEnable, ThousandthsCarryOut, HundredthsCarryOut, TenthsCarryOut, SecondsCarryOut, DisplayCou...ytes[3:0], DisplayCounter[1:0], ClkDisplayOut, cur_counter[3:0], TimerOverflow, Clear_out, Enable_out_out, counter_10...carry_out, sel[1:0], data[3:0], timer_count, millisecondEnable, Clk, Reset, Button, EoC_rand, clear, enable, and a signal with a value of 881.
- Main Display Area:** A waveform view showing digital signals over time. The time axis ranges from 9,965 us to 10,010 us. A vertical yellow line is positioned at 10,008.836083 us. The signal 'CounterVal...ths[3:0]' is highlighted in blue and shows a sequence of values: 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, 0, 1, 2, 3.
- Signal List (Right):** A list of signals including MAX_COUNT, OUT_MAX[3:0], Reset, Clk, Enable, an[3:0], [3], [2], [1], [0], seg[6:0], CounterEnable, CounterValueMs[3:0], CounterVal...ths[3:0] (highlighted), CounterVa...onds[3:0], SecondsEnable, TenthsEnable, HundredthsEnable, ThousandthsCarryOut, HundredthsCarryOut, TenthsCarryOut, SecondsCarryOut, DisplayCou...ytes[3:0], DisplayCounter[1:0], ClkDisplayOut, cur_counter[3:0], TimerOverflow, Clear_out, Enable_out_out, counter_10...carry_out, sel[1:0], data[3:0], timer_count, millisecondEnable, Clk, Reset, Button, EoC_rand, clear, enable, and a signal with a value of 881.

When the random timer reaches its 1 second the counter starts counting and will continue to count until the button is pressed again.